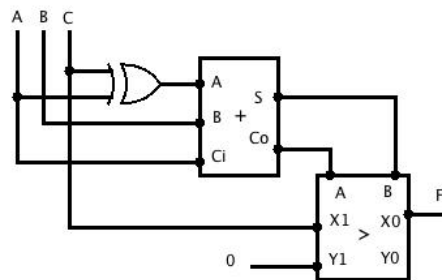


Digital Systems

Combinatorial circuits

1. Implement a complete 1 bit adder circuit in Logisim. Using that circuit, build an adder circuit of 4 bits.
2. Implement a 1 bit comparator circuit in Logisim. Using that circuit, build a comparator of 4 bits.
3. Simplify the function $F(A, B, C)$, represented by the circuit in the following picture:



4. Implement the function $F(A, B, C, D, E, F)$ using combinatorial circuits, where F is defined by:

$$F(A, B, C, D, E, F) = \begin{cases} A > B & \text{if } C = 1 \\ D & \text{if } C = 0 \text{ and } (E + F) > 1 \\ (E + F) > 1 & \text{otherwise} \end{cases}$$

(the + symbol represents the sum operation and not the usual *OR*.)

5. Project and build a circuit that converts code X to binary according to the following table.

Code X	Decimal
0011	0
0101	1
0110	2
1001	3
1010	4
1100	5

6. Build the circuit that implements the function $F(A, B, C, D, E, F, G)$ that only takes value 1 when the input variables with value 1 is pair.
7. Consider that you have a 7 segment display (a,b,c,d,e,f):
 - (a) Draw the circuit that decodes binary to hexadecimal.
 - (b) Repeat last exercise (7a) using the “Combinatorial Analysis” of LogiSim and compare the results.
 - (c) Complete the circuit in the simulator and verify if it’s working.
8. Implement in LogiSim the 4x2 priority encoder circuit presented in the theoretical class. Expand that circuit for an 8 input encoder and check how it works.