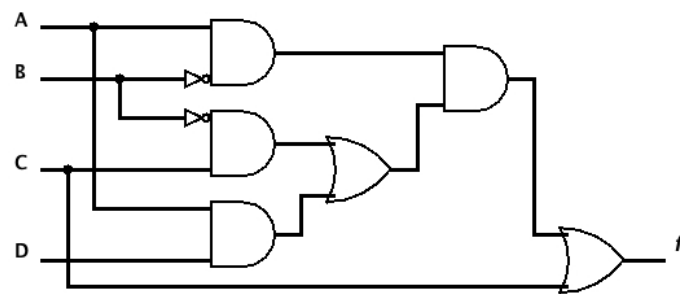


Digital Systems

Representation and simplification of functions

1. Using gates AND, OR and NOT, draw the simplified functions that you obtained in exercise 2 of from exercise sheet 3 – “Binary functions and Boole algebra”.
2. Given the following logical circuit:



- (a) Define the function $f(A, B, C, D)$
 - (b) Simplify the function
 - (c) Draw the logical circuit of the simplified function
3. For the function defined in exercise 5 of exercise sheet 3 – “Binary functions and Boole algebra”, draw the logical circuit using:
 - (a) gates AND, OR and NOT
 - (b) gates NAND
 - (c) gate NOR

4. Consider the following truth table

A	B	C	$f(A, B, C)$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- Write the function $f(A, B, C)$ in the canonical form AND-OR, using the decimal symbology
 - Represent the function using a Karnaugh map
 - Use the map to simplify the function in the form AND-OR
 - Use the map to simplify the function in the form OR-AND
5. Using Karnaugh maps, simplify the following functions using the forms AND-OR and AND-AND:
- $F(A, B, C, D) = \sum m(4, 5, 8, 12, 13, 14, 15)$
 - $F(A, B, C, D) = \prod M(2, 3, 6, 7, 10, 12, 13, 14)$
 - $F(A, B, C, D) = (A + \overline{B} + C) \cdot (\overline{A} + D) \cdot (B + C + \overline{D})$
 - $F(A, B, C, D) = \overline{A} C \overline{B} + A D + B \overline{D} + C \overline{D} + A \overline{C} + \overline{A} \overline{B}$
6. Interpret the following Karnaugh map and simplify the function using the forms AND and OR-AND:

					<u>A</u>									
					<u>E</u>									
B		-	1	1	-		C	1	1	1	-		B	
		0	-	1	-			1	1	-	1			
		-	-	-	-			0	-	-	-			
		0	1	1	1			0	-	1	1			
					<u>D</u>									

7. Using the “bridging” method, implement the function $F(A, B, C) = \prod(1, 4, 5, 6)$, using as component the function $G(A, B, C) = A \overline{B} + B C$.