

# Digital Systems

## Representation and simplification of functions

### proposed exercises<sup>1</sup>

1. Consider the function  $F$  defined by expression  $F = A\overline{D} + B\overline{C} + \overline{A}BD + ABCD + \overline{A}BC\overline{D}$ .
  - (a) Draw the logic diagram of  $F$ .
  - (b) Simplify the function and draw the corresponding logical diagram.
  - (c) Compare the two implementations and comment the need for simplifying the functions.
2. Consider the function  $f(A, B, C, D) = ABC + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}D + \overline{B} \overline{C} \overline{D}$ .
  - (a) Simplify the function using Karnaugh maps.
  - (b) Implement the function using only NOR gates.
  - (c) Draw the logic diagram of the function.
3. A project team is studying the selection of a new network server. Since it received many proposals, the team wants an automatic system to select the quality of each proposal. The team determined that there are 5 options in the equipment:
  - option A has the weight of 30%
  - options B and C have the weight of 20%
  - options D and E have the weight of 15%

If the quality of the proposal is higher or equal than 70%, the recommendation is to buy it; if the quality of is lower than 70%, but higher than 50%, the decision is indifferent; if the quality is lower than 50%, the proposal is rejected.

  - (a) Using a truth table, represent the function that corresponds to the requirements of the team project.
  - (b) Simplify the function.
  - (c) Draw the logical diagram of the simplified functions
4. Consider the function  $f(A, B, C, D) = \sum m(1, 3, 8, 10, 13, 14, 15) + i(0, 2)$ , where  $i()$  indicates the indifferences of the functions.
  - (a) Indicate the maxterms.
  - (b) Simplify the function.
  - (c) Implement the simplified function using only NAND gates.

---

<sup>1</sup>Adapted from the book *Sistemas Digitais, princípios e prática*. Morgado Dias. FCA, 2010.

(d) Implement the simplified function using only NOR gates.

5. Consider the following Karnaugh map of function  $G$  and simplify it:

Diagram illustrating a 4x4 grid structure with dimensions  $a$ ,  $b$ ,  $c$ , and  $d$ . The grid is labeled  $E = 0$  below it.

1	0	0	1
0	0	0	0
0	0	1	1
0	1	1	1

Diagram illustrating a 4x4 grid structure. The grid is labeled with dimensions  $a$  (height),  $b$  (width),  $c$  (width), and  $d$  (width). The grid contains the following values:

1	0	0	1
1	0	0	0
0	0	0	1
1	0	0	1

The value  $E = 1$  is indicated below the grid.