

Sistemas Digitais

Sequential Synchronous Circuits

1. The XY edge-triggered flip-flop keeps the state 0 if $X=0$ and in state 1 if $Y=1$, changes from 0 to 1 if $X=1$ and from 1 to 0 if $Y=0$.
 - (a) Draw the state transition table for flip-flop XY
 - (b) Draw the state diagram (ASM model)
 - (c) Project the flip-flop XY with
 - i. a flip-flop JK
 - ii. a flip-flop T
 - iii. a flip-flop D
2. Project the circuit that generates the sequence presented in Figure 1, using edge-triggered flip-flops D.

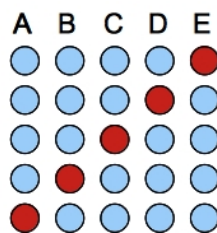


Figure 1: Sequence to be generated

3. Figure 2 represents the state transition diagram of a sequential circuit. Using flip-flops T, project the circuit e describe its behavior.
4. Using flip-flops T, project and implement a circuit that presents the value **1** as output when the sequence **110010** is detected.
5. Project um module 7 counter using:
 - (a) flip-flops D
 - (b) flip-flops JK
6. Consider the circuit of Figure 3.
 - (a) Simplify the function.

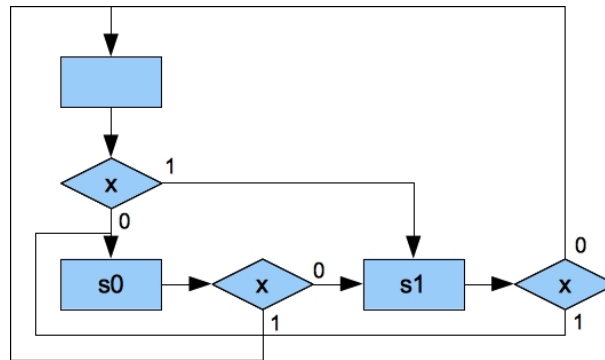


Figure 2: Diagrama de estados de um circuito sequencial síncrono

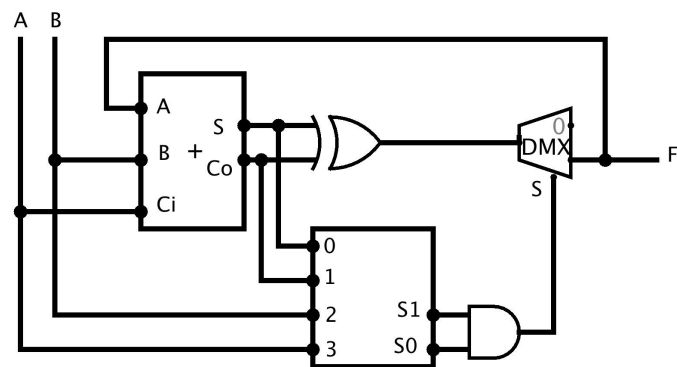


Figure 3: Sequential circuit

- (b) Draw the state transition table.
 - (c) Draw the state transition diagram.
 - (d) Implement the function F using flip-flops SR.
7. Project a module 4 counter that generates the sequence 3, 6, 1, 4 using flip-flops D.
8. A de-pressurization system of a submarine is made of a motor (M) that levels the pressure existent on the inside and in the outside, by a pressure sensor (PS) that has the value 1 when the pressure is leveled, and by a sensor (DC) that has the value 1 when all doors are closed. The motor is only actuated when all doors are closed and it stops when the pressure is leveled.
- (a) Draw the ASM model of the circuit and state transition table.
 - (b) Draw the corresponding sequential circuit using flip-flops D.